

Voltage across the battery is  $V$ . It goes from 0 to  $V_{dd}$  in time say  $T$ . so the slope is  $\frac{V_{dd}}{T}$

Voltage across battery is  $\frac{V_{dd}}{T}t$ .

Energy supplied by battery is

$$\int_0^T v i dt = \int_0^T v c \frac{dv}{dt} dt = \left(\frac{V_{dd}}{T}\right)^2 c \int_0^T t dt = \frac{1}{2} C V_{dd}^2$$

This is actually the energy stored in the capacitor. if  $T$  tends to zero the result will remain the same.

as anyway the voltage has to change from 0 to  $V_{dd}$  in zero seconds..