
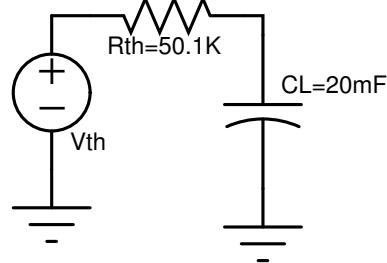


**Figure 1:** Noise with voltage source

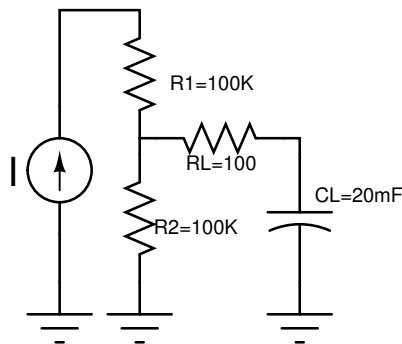

**Figure 2:** Thevenin Equivalent with load  $C_L$



**Figure 3:** Noise with Current source

PSD of each resistor is given as

$$S_{R1} = 4KTR_1 = 4 * 1.38 * 10^{-23} * 300 * 100K = 1.66 * 10^{15} V^2/Hz = S_{R2}$$

$$S_{RL} = 4 * 1.38 * 10^{-23} * 300 * 100 = 1.66 * 10^{18} V^2/Hz$$

$$S_{total}^1 = \frac{S_{R1}}{4} + \frac{S_{R2}}{4} + S_{RL} = 8.32 * 10^{-16} V^2/Hz$$

Thevenin equivalent noise voltage density =  $V_{th} = \sqrt{S_{total}}$  = 28.83n V/ $\sqrt{Hz}$

Thevenin resistance =  $R_{th} = 100K \parallel 100K + 100 = 50.1K \Omega$

Output noise voltage density across  $C_L$  =  $V_{OUT} = \frac{V_{th}}{1+j\omega R_{th} C_L} = 4.57 * 10^{-12} \angle -89.9 V/\sqrt{Hz}$

**Noise current through  $C_L$**  =  $V_{OUT} * j * \omega * C_L = 574 * 10^{-15} \angle 9.1m A/\sqrt{Hz}$

Spice code for setup 1 is given below

```

V1 1 0 AC 1 DC 5
R1 1 2 100K
R2 2 0 100K
RL 2 3 100
CL 3 0 0.02
.AC DEC 8 1 100MEG

```

---

<sup>1</sup>CL is disconnected for calculating total PSD and for thevenin equivalent.

```
.NOISE V(3) V1 5  
.PRINT NOISE ONOISE  
.PROBE  
.END
```

For measuring noise current

```
.NOISE V(3) V1 5
```

is replaced by statement

```
.NOISE I(C1) V1 5
```

Spice code for setup 3 is given below

```
I1 1 0 ac 100m dc 10m  
R1 1 2 100K  
R2 2 0 100K  
RL 2 3 100  
CL 3 0 0.02  
.AC DEC 8 1 100MEG  
.NOISE I(CL) I1 5  
.PRINT NOISE ONOISE  
.PROBE  
.END
```