

Figure 1: Middlebrook Voltage Loop Gain, T_v , and Middlebrook Current Loop Gain, T_i

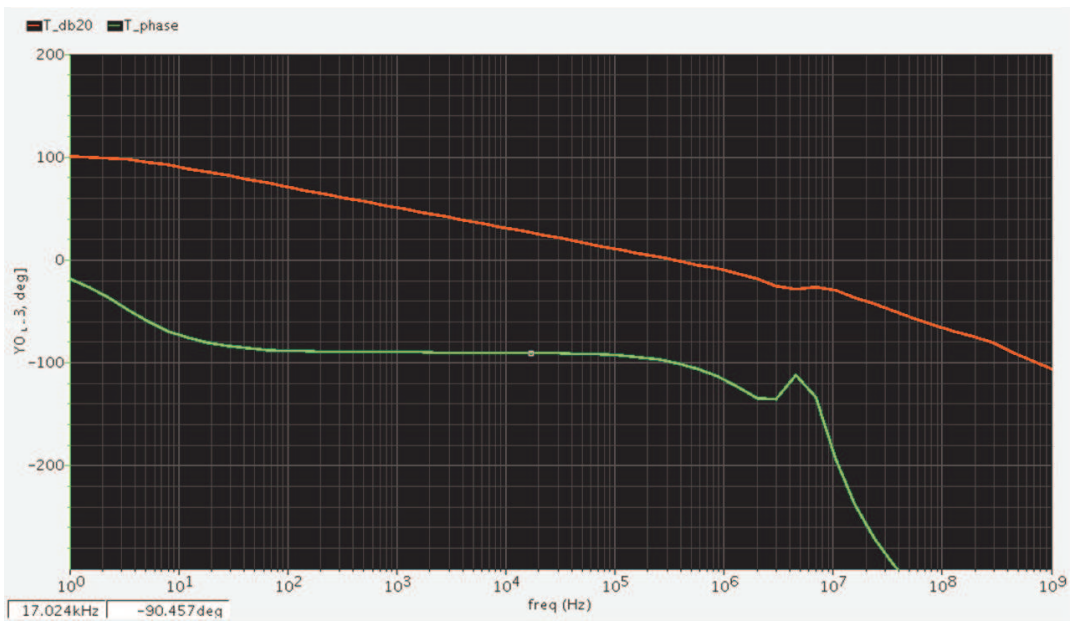


Figure 2: Middlebrook Composite Loop Gain