

# Design of MOS Amplifiers Using gm/ID Methodology

Ashutosh Tiwari

# Outline

- Introduction
- Why gm/Id Methodology
- Performance Metrics
- Generation Of Performance Curves
- Implementation And Design examples

# Introduction

Mainstream methods assume generally strong inversion and use the transistor gate voltage overdrive ( $V_{ov}$ ) as the key parameter. Micropower design techniques, on the other hand, exploit weak inversion models.

This methodology is based on a unified synthesis methodology in all the regions of operation of MOS transistor.

# Introduction



- The method exploits the transconductance over dc drain current ratio ( $g_m/I_d$ ) relationship versus the normalized current [ $I_d/(W/L)$ ].

# Why gm/Id Methodology

Consider a simple common source amplifier, the power and bandwidth are given by following equations:

$$P = \frac{1}{2} \frac{V_{DD}}{R_L} \cdot A_{DC} \cdot V_{OV}$$

$$\omega_{-3dB} = \frac{3 R_L}{2 R_i} \cdot \frac{1}{A_{DC}} \cdot \frac{\mu}{L^2} \cdot V_{OV}$$


$$\frac{W}{L} = \frac{g_m}{\mu C_{ox} V_{OV}}$$

With  $g_m$  and  $L$  fixed, smaller  $V_{OV}$  translates into a bigger (wider) device, and thus larger  $C_{gs}$ . So we conclude from this that the  $V_{OV}$  is not a good design parameter

# Why gm/Id Methodology

The choice of gm/Id is based on its relevance for the three following reasons:

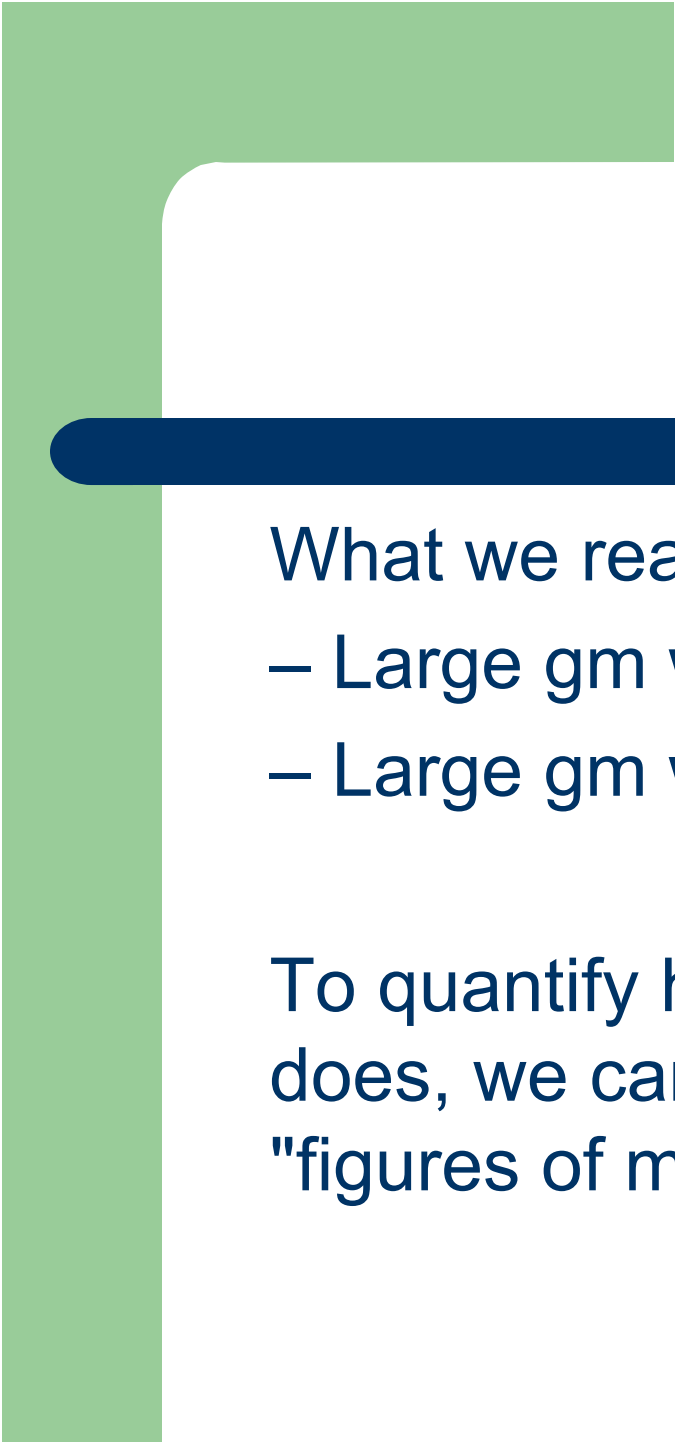

1. It is strongly related to the performances of analog circuits.
2. It gives an indication of device operating region.
3. It provides a tool for calculating the transistors dimensions.

## How gm/Id is an indicator of the mode of operation?

$$\frac{g_m}{I_D} = \frac{1}{I_D} \frac{\partial I_D}{\partial V_G} = \frac{\partial(\ln I_D)}{\partial V_G} = \frac{\partial \left\{ \ln \left[ \frac{I_D}{\left(\frac{W}{L}\right)} \right] \right\}}{\partial V_G}$$

This derivative is maximum in weak inversion region. The gm/Id ratio decreases as the operating point moves toward strong inversion.



- 
- 
- What we really want from MOS transistor
- Large  $g_m$  without investing much current
  - Large  $g_m$  without having large  $C_{gs}$

To quantify how good of a job our transistor does, we can therefore define the following "figures of merit":

# Performance Metrics of Interest:

- Transit Frequency: (or Unity Gain Frequency)

$$\omega_T = \frac{g_m}{C_{gs}}$$

It is the maximum frequency beyond which MOS transistor will not act as amplifier.

- Intrinsic Gain:


$$g_m r_o$$

- Trans-conductor Efficiency: (Should be high)  
It is the efficiency of the MOS transistor to translate given current into an equivalent transconductance.

$$\frac{g_m}{I_D}$$


# Generation of Performance Curves

## gm/ID Simulation

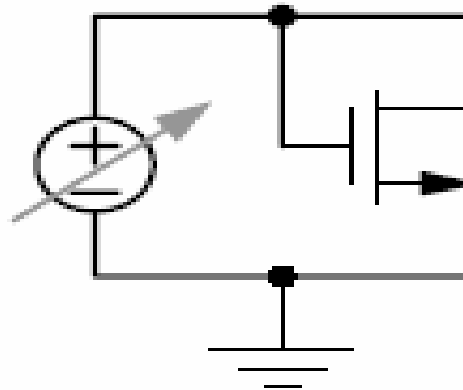


Ashutosh Tiwari

# gm/ID Vs Vov curve

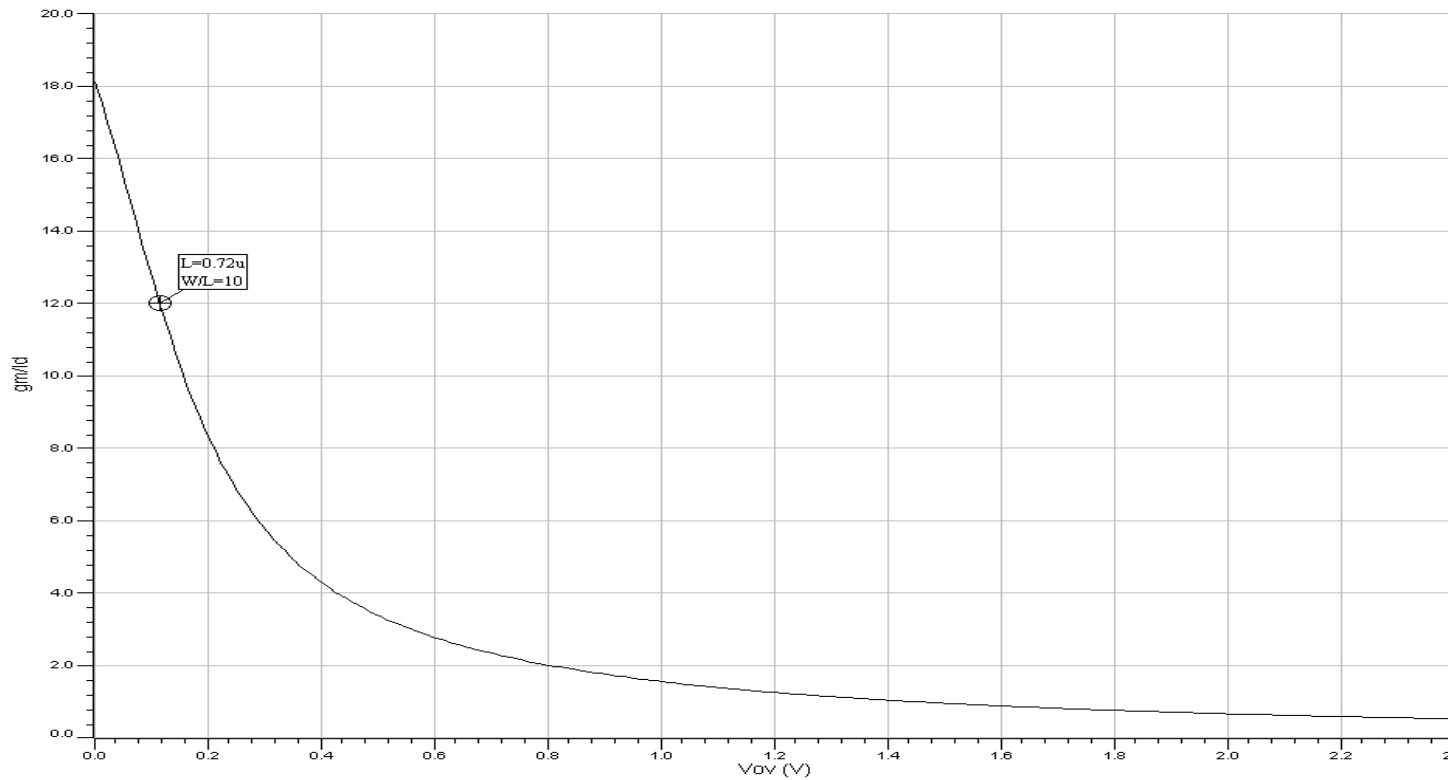


gm\_by\_id\_072 (v

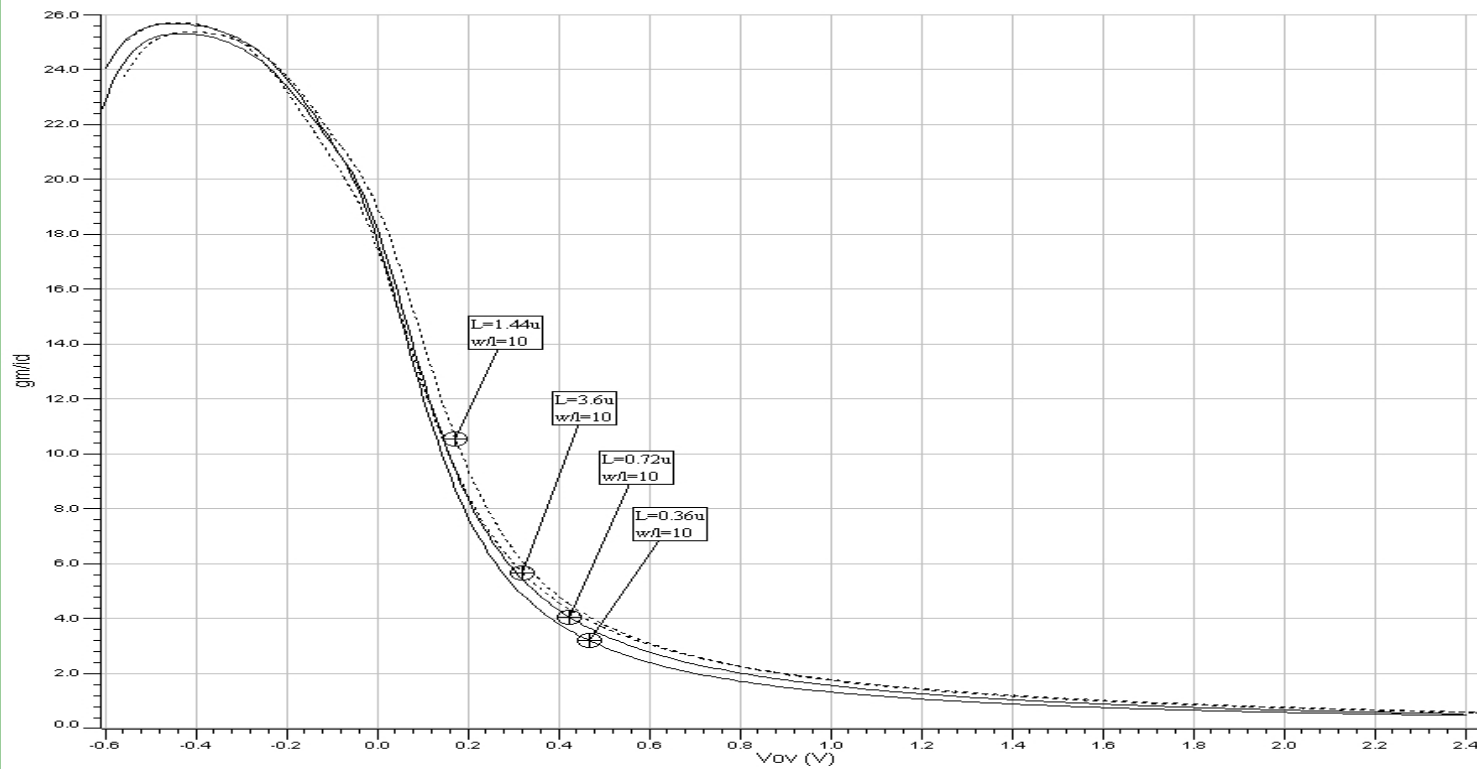


id vs Vov\_L306  
id vs Vov\_L036  
id vs Vov\_L144  
id vs Vov\_L072

Ashutosh Tiwari

# ID/(W/L) Vs gm/ID curve

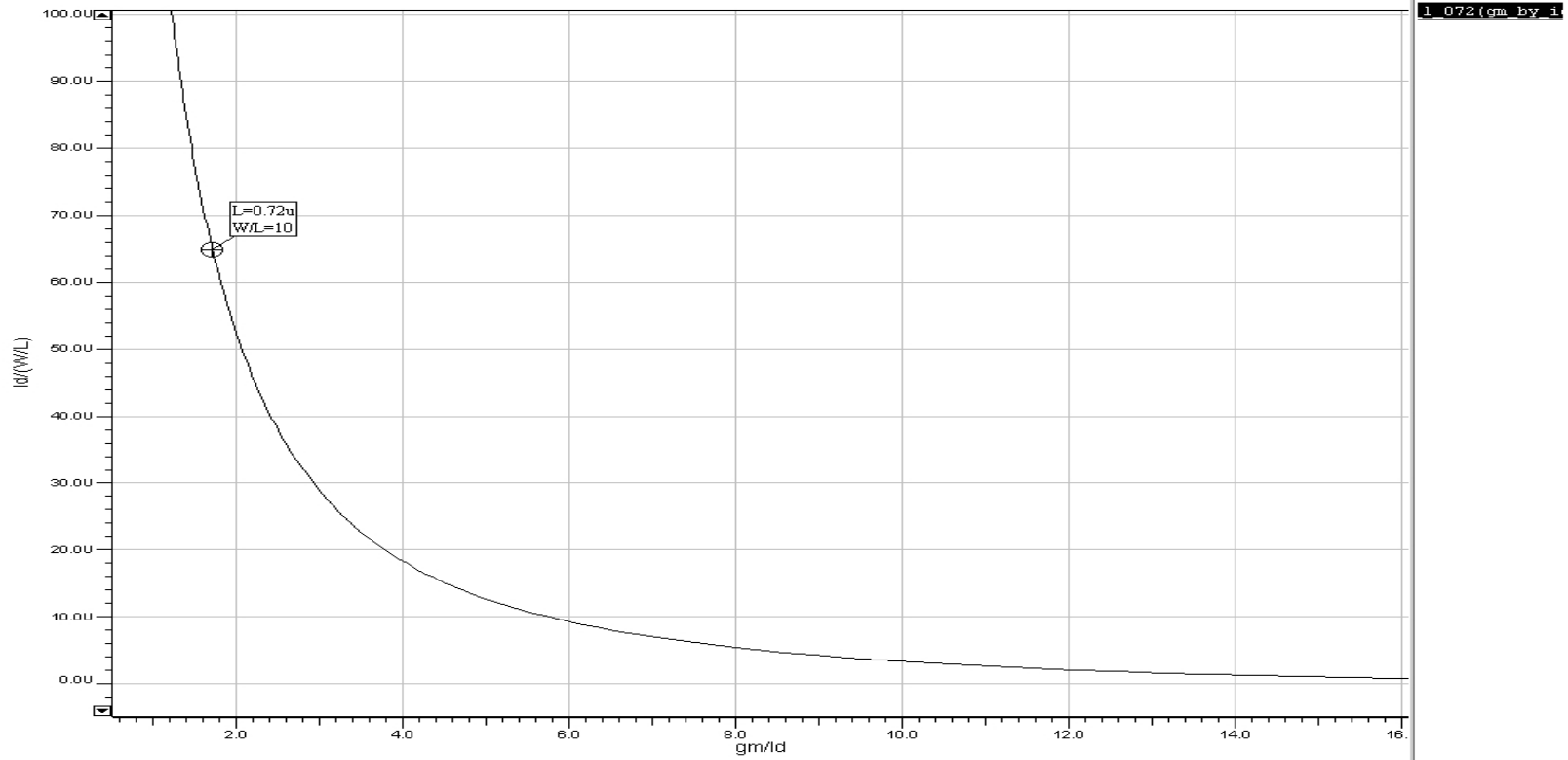

Ashutosh Tiwari

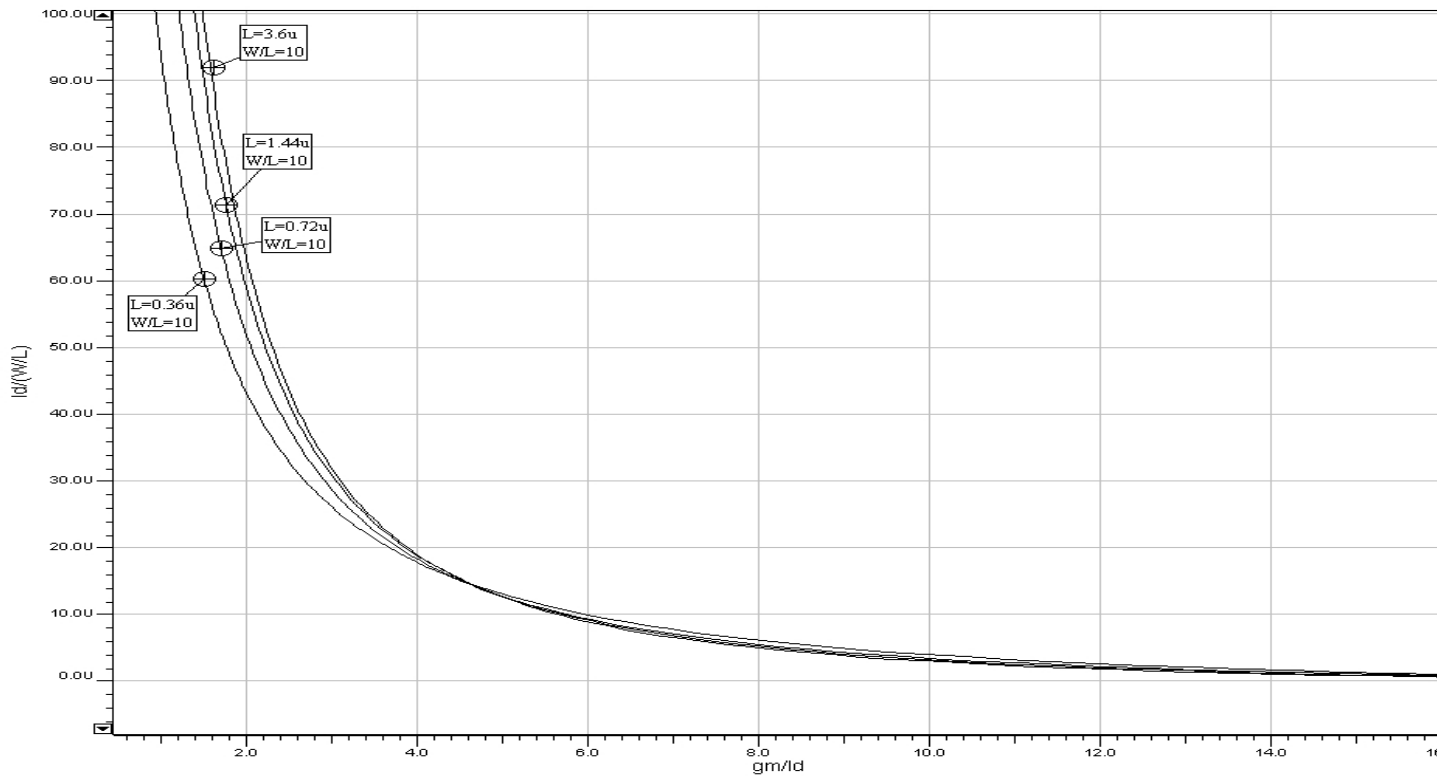


(gm\_by\_id\_036)  
 (gm\_by\_id\_072)  
 (gm\_by\_id\_144)  
 5(gm\_by\_id\_36)

Ashutosh Tiwari




# ft Simulation

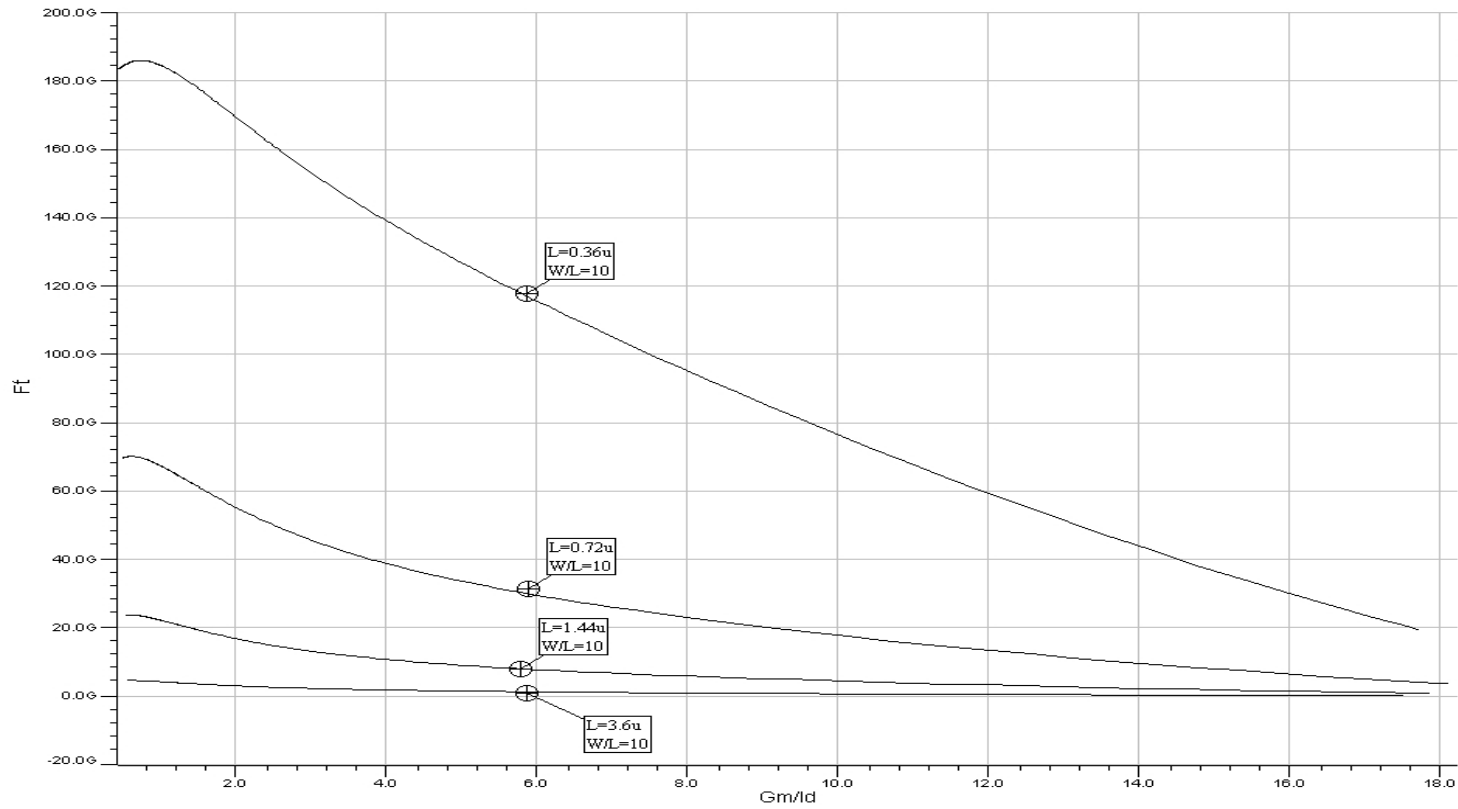

ft\_036(gm\_by\_i  
ft\_072(gm\_by\_i  
ft\_144(gm\_by\_i  
ft\_36(gm\_by\_ic


Ashutosh Tiwari

# Intrinsic Gain Simulation

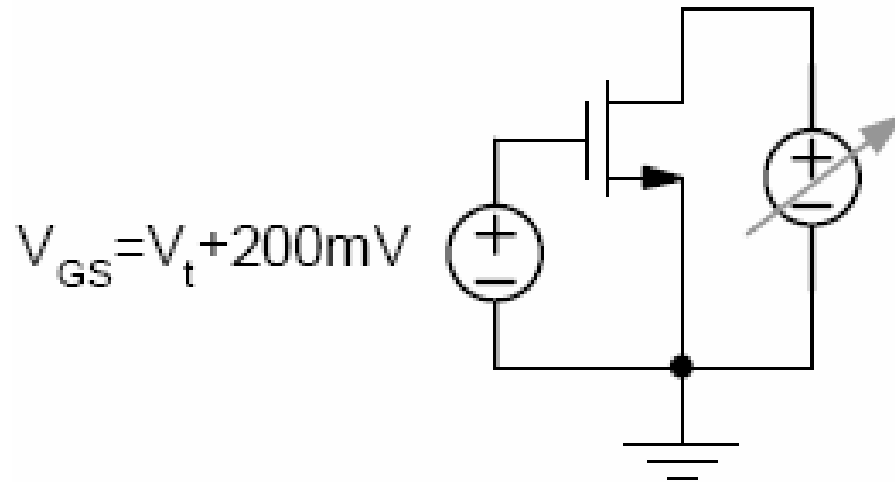

Ashutosh Tiwari


# Gmxro Vs Vds Curve

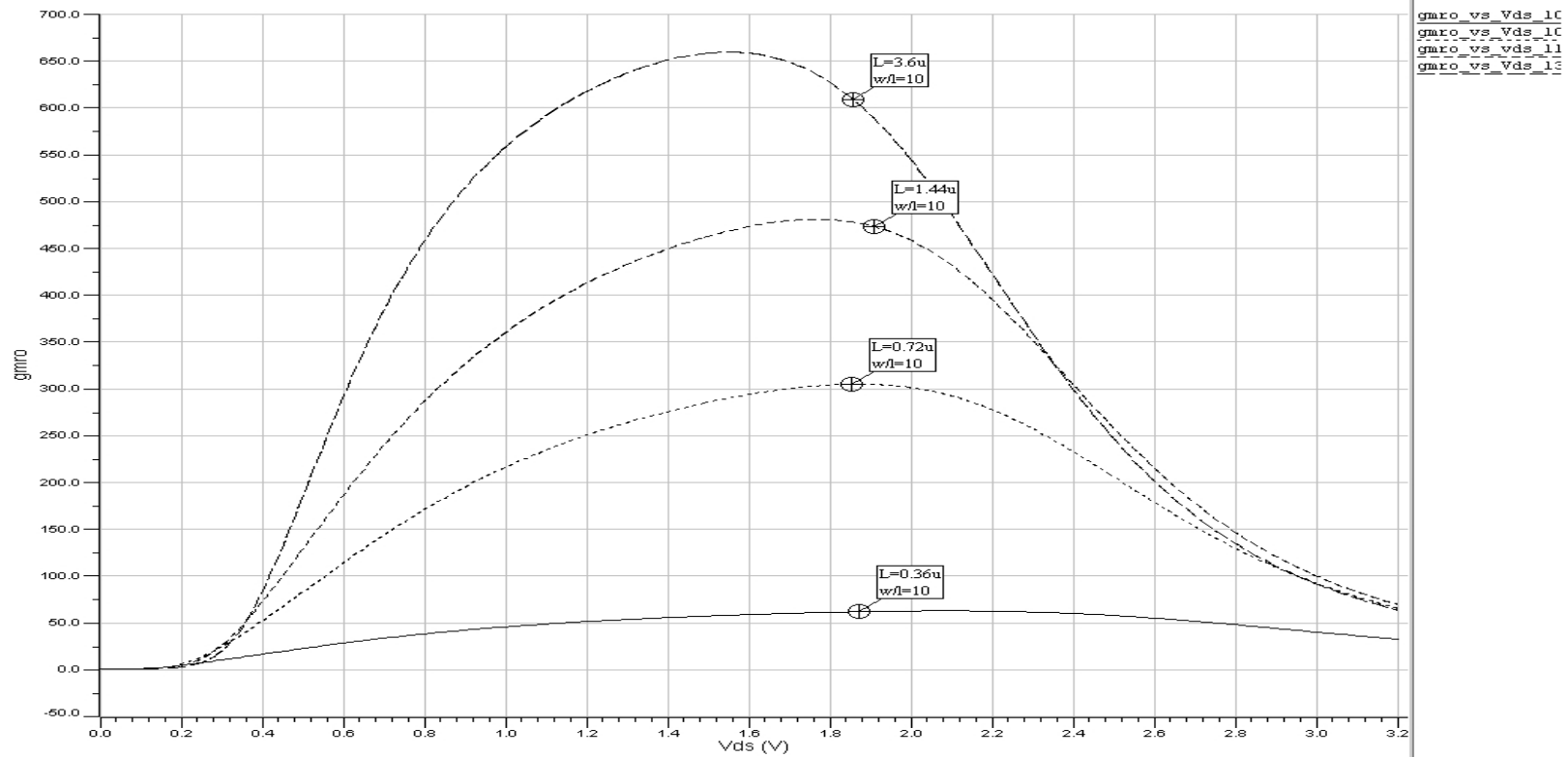

gmro vs Vds\_10  
gmro vs Vds\_10  
gmro vs vds\_11  
gmro vs Vds\_13

Ashutosh Tiwari

# Design Example:

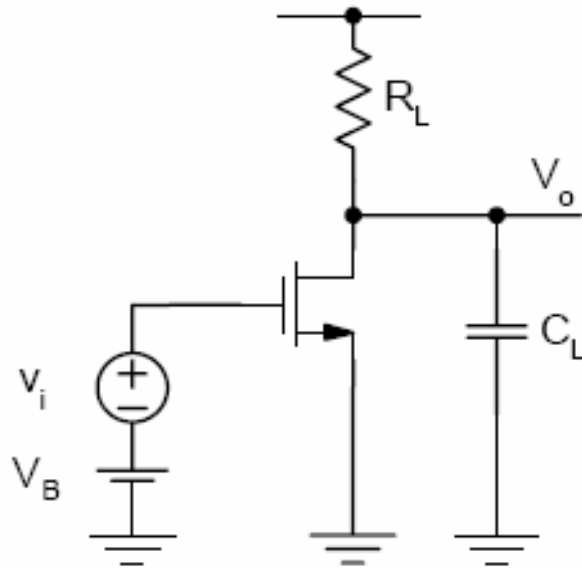

Given specifications

– DC gain=-2,  $I_D \leq 1\text{mA}$ ,  $f_{-3\text{dB}}=100\text{MHz}$ ,  $C_L=10\text{pF}$

Ashutosh Tiwari

## Solution:

– From the given specifications, we can find  $g_m$  and  $R_L$  as follows:

$$f_{-3dB} = \frac{1}{2\pi R_L C_L} \Rightarrow R_L = \frac{1}{2\pi \cdot 100\text{MHz} \cdot 10\text{pF}} = 159\Omega$$

$$A_{DC} = -g_m R_L = -2 \Rightarrow g_m = \frac{2}{159\Omega} = 12.6\text{mS}$$


- With the maximum available current, we have
$$g_m/I_D = 6.3 \text{ V}^{-1}$$
- From the current density chart, we can find out  $I_D/(W/L)$  for the corresponding  $g_m/I_D$ .
$$I_D/(W/L) = ?$$
- Get  $V_{ov}$  corresponding to  $g_m/I_D$  from  $g_m/I_D$  Vs  $V_{ov}$  chart

$$V_{ov} \cong ?$$

From this we get the device  $W$  as

$$W = I_D * L$$
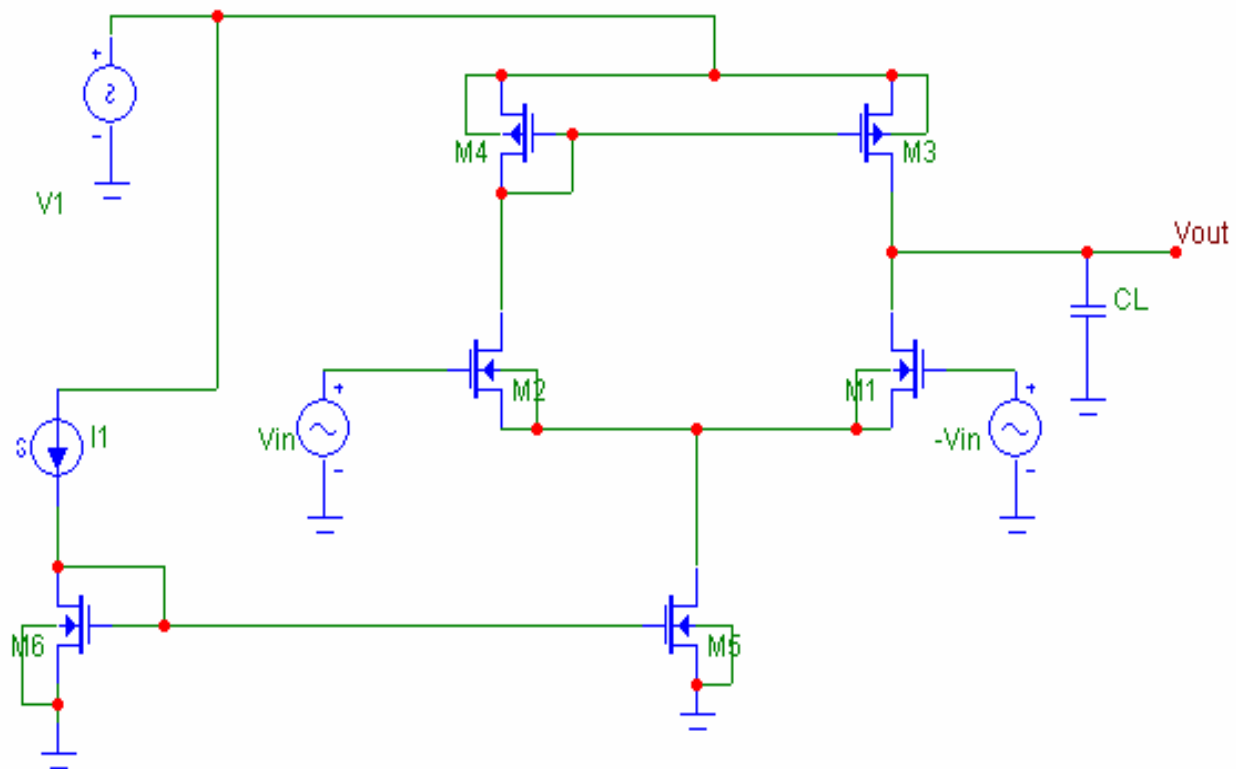
# Design Example: Differential Amplifier (Single Ended Output)



Ashutosh Tiwari



Thank You

?

Ashutosh Tiwari



# References

- D. Flandre, A. Viviani, J.-P. Eggermont, P. Jespers, "Improved synthesis of regulated-cascode gain-boosting CMOS stage using symbolic analysis and gm/ID methodology", *IEEE Journal of Solid-State Circuits* (Special Issue on 22<sup>nd</sup> ESSCIRC conference), 32 (1997) 1006-1012.
- Silveira F., Flandre D., Jespers P.G.A. *A gm/ID based methodology for the design of CMOS analog circuits and its application to the synthesis of a silicon-ion- insulator micropower OTA*. *IEEE Journal of Solid State Circuits*. Vol. 31, pg 1314-1319, Sept. 1996.