



$$\frac{V_o}{V_1} = \frac{R_2 \parallel R_3}{(R_2 \parallel R_3) + R_1} = \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = k_1 = 1 \quad (1)$$

$$\frac{V_o}{V_2} = \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = k_2 = 2.5 \quad (2)$$

$$\frac{V_o}{V_3} = \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} = k_3 = 3 \quad (3)$$

$$\frac{V_o}{-v_{fb}} = G_m \left(\frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right) = 2 \quad (4)$$

$$\left. \begin{array}{l} \text{from (1) \& (2)} \\ \text{from (1) \& (3)} \end{array} \right\} \begin{array}{l} \frac{R_1}{R_2} = 2.5 \\ \frac{R_1}{R_3} = 3 \end{array} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} R_1 = 2.5 R_2 \\ R_1 = 3 R_3 \end{array}$$

$$\text{if } R_1 = 15 \text{ k}\Omega \Rightarrow \left\{ \begin{array}{l} R_2 = 6 \text{ k}\Omega \\ R_3 = 5 \text{ k}\Omega \end{array} \right.$$

So,

R_1	R_2	R_3
$15 \text{ k}\Omega$	$6 \text{ k}\Omega$	$5 \text{ k}\Omega$

$$\text{from (4)} \quad G_m \left(\frac{15 \times 6 \times 5}{90 + 30 + 75} \right) = 2$$

$$G_m = 0.8666 \text{ mS}$$

if we plug in $R_1 R_2 R_3$ to (1) (or) (2) (or) (3)

$$\text{for example (1)} \Rightarrow \frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{30}{195} = 0.1538 \quad (5)$$

$$\text{for example (2)} \Rightarrow \frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{75}{195} = 0.3846 \quad (6)$$

$$\text{and (3)} \Rightarrow \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{90}{195} = 0.4615 \quad (7)$$

if (5)/(6)/(7) $\times 6.5 \Rightarrow$ correct coefficients